

# Princess Sumaya University for Technology

The King Abdullah II School for Electrical Engineering  
Electronics Engineering Department

## Digital Electronics Lab

In Lab Report

Experiment 10:

### Introduction to VERILOG (2)

Names of Group: 1. .... ID#:.....  
2. .... ID#:.....  
3. .... ID#:.....

Group No.:

Section:


Date:        /        /

## Objectives

1. ....
2. ....

### A) Basic Logic Gates

 
1. Draw a Moore FSM that describes an odd parity checker (assert when number of 1s is odd)



2. Write down the VERILOG code for a tri-state buffer and the testbench code to test it.

--	--


2. Draw the resulting waveform

 

2. Write down the VERILOG code for a 4-input multiplexer and the testbench code to test it.

--	--

2. Draw the resulting waveform

 

2. Write down the VERILOG code for a 2-to-4 decoder and the testbench code to test it.

--	--

2. Draw the resulting waveform

