

Digital Electronics Laboratory Project

Using Verilog, **design the following:**

1. A module for 2-input AND
2. A module for 2-input OR
3. A module for a 2-input XOR

Using the above modules, Design a 2-bit full subtractor as seen below:


Provide your verilog code+ testbench file + simulations for each part.

- Submit your work using the **full-report template**.
- **Deadline for Online Submission:** 2 Jan. 2026 (4:00 p.m.)

- **For simplicity:**
Inputs and Outputs:

- **Inputs:**
 - A: Minuend (1-bit)
 - B: Subtrahend (1-bit)
 - Bin: Borrow-in (1-bit)
- **Outputs:**
 - Diff: Difference (1-bit)
 - Bout: Borrow-out (1-bit)
- **Truth Table:**

Input			Output	
A	B	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 

Full Subtractor using XOR, NOT, AND, OR logic gates